

31. A choke is used as a resistance in

  - A. DC circuit
  - B. AC circuits
  - C. Both AC and DC circuit
  - D. Full wave rectifier circuit

**Answer:** Option B

32. At resonance the value of the power factor in an L-C-R series circuit is

  - A. Zero
  - C. 1
  - D. not definite

**Answer:** Option C

33. An A.C series circuit containing 4? resistance and 3-? inductive reactance. The impedance of the circuit is

A. 1?  
B. 5?  
C. 7?  
D.  $7/\sqrt{2}?$

**Answer:** Option B

34. An inductive coil has a resistance of 100Ω. When an AC signal of frequency 1000Hz is fed to the coil the applied voltage leads the current by 45°. What is the inductance of the coil?

A. 10mH            B. 12mH  
C. 16mH            D. 20mH

**Answer:** Option C

35. Choose the correct statement. In the case of AC circuit ohms law holds for

  - A. Peak values of voltage and current
  - B. Effective values of voltage and current
  - C. Instantaneous values of voltage and current
  - D. All of the above

**Answer:** Option D

36. The phase angle between the voltage and the current in an AC circuit consisting of a resistance is

- |                |                |
|----------------|----------------|
| <u>A.</u> Zero | <u>B.</u> 45?  |
| <u>C.</u> 90?  | <u>D.</u> 180? |

**Answer:** Option A

37. In an LCR series circuit, if V is the effective value of the applied voltage VR is the voltage across R VL is the effective voltage across L & Vc is the effective voltage across C then

- |                                      |                                      |
|--------------------------------------|--------------------------------------|
| <u>A.</u> $V = VR + VL + VC$         | <u>B.</u> $V^2 = VR^2 + VL^2 + VC^2$ |
| <u>C.</u> $V^2 = VR^2 + (VL - VC)^2$ | <u>D.</u> $V^2 = VL^2 + (VR - VC)^2$ |

**Answer:** Option C

38. a voltage  $V = V_0 \cos \omega t$  is applied across a resistor of resistance R the average power dissipated per cycle in the resistor is given by

- |                        |                              |
|------------------------|------------------------------|
| <u>A.</u> $V_0^2 / 2R$ | <u>B.</u> $V_0^2 / 2\pi R$   |
| <u>C.</u> $V_0^2 / 2R$ | <u>D.</u> $V_0^2 / 2\pi^2 R$ |

**Answer:** Option C

39. Two identical coaxial circular loops carry equal currents in the same direction. If the loops approach each other the current in

- |                                 |   |
|---------------------------------|---|
| <u>A.</u> Each increases        | <u>B.</u> Each decreases                                    |
| <u>C.</u> Each remains the same | <u>D.</u> One increases whereas that in the other decreases |

**Answer:** Option B

40. An inductor may store energy in

- |                              |                     |
|------------------------------|---------------------|
| <u>A.</u> its electric field | <u>B.</u> its coils |
|------------------------------|---------------------|

C. its magnetic field

D. both electric and magnetic fields

**Answer:** Option C